

Figure 2. Mode of Operation of NCP1601

**DESIGN STEPS**

**Step 1. Define the Specifications**

Table 1. Specifications

Input	85 Vac to 265 Vac, 50 Hz
Output	100 W, 390 Vdc
Switching frequency	Around 100 kHz

The maximum overvoltage threshold is limited to 225  $\mu$ A which corresponds to 225  $\mu$ A  $\times$  1.95 M $\Omega$  + 5 V = 443.75 V when feedback resistor R<sub>FB</sub> is 1.95 M $\Omega$  (1.8 M $\Omega$  + 150 k $\Omega$ ) and a 5 V maximum offset of the feedback pin of the NCP1601. Hence, a 450 V output capacitor can be used in the output of the circuit. Then, the nominal output voltage is set at 390 V.

$$V_{out} = 200 \mu \times 1.95 M\Omega = 390 V$$

**Step 2. Bias Supply Design**

A 1/2 W axial 150 k $\Omega$  resistor is used to charge up the V<sub>CC</sub> capacitor in startup. The worst case power dissipation on this resistor is 0.47 W which is smaller than 1/2 W.

$$Power = \frac{V^2}{R} = \frac{265^2}{150 \times 10^3} = 0.47 W$$

 


Figure 3. Auxiliary Winding Bias Supply.

The auxiliary winding bias supply in Figure 3 is to provide a V<sub>CC</sub> bias voltage after startup. The V<sub>CC</sub> needs to be higher than its minimum operating voltage V<sub>CC(off)</sub> (9 V typical). When the PFC stage MOSFET is on, the primary winding is

with a voltage V<sub>in</sub> and the secondary winding is with a voltage V<sub>in</sub> / n. This voltage goes to capacitor C<sub>1</sub>. When the PFC stage diode is on, the primary winding is with a voltage (V<sub>out</sub> - V<sub>in</sub>) and the secondary winding is with a voltage (V<sub>out</sub> - V<sub>in</sub>) / n. This voltage goes to capacitor C<sub>2</sub>. As a result, the V<sub>CC</sub> biasing voltage will be V<sub>out</sub> / n which is almost constant and independent of the 50 Hz variation of the input voltage.

$$V_{CC} = V_{C1} + V_{C2} = \frac{V_{in}}{n} + \frac{V_{out} - V_{in}}{n}$$

$$= \frac{V_{out}}{n} > V_{CC(off)}$$

Hence, the auxiliary winding turn ratio n is selected as 25:1 so that V<sub>CC</sub> is 15.6 V.

$$V_{CC} = \frac{V_{out}}{n} = \frac{390}{25} = 15.6 V$$

A 470  $\mu$ F V<sub>CC</sub> capacitor is experimentally found to be enough for the circuit startup transient t<sub>start</sub> = 893 ms in the worst case of 85 Vac input given that it consumes typical 2.5 mA for an UVLO margin 4.75 V in NCP1601A.

$$t_{start} = \frac{CdV}{I} = \frac{470 \times 10^{-6} \cdot 4.75}{2.5 \times 10^{-3}} = 893 ms$$

For protection purpose, a clamping Zener MZP4745A is added to prevent any unwanted transient overvoltage damage.

It is noted that the circuit needs typical 11.4 sec to let the V<sub>CC</sub> capacitor reach the starting threshold (13.75 typical) in the worst condition V<sub>in</sub> = 85 Vac.

$$t_{start} = \frac{CdV}{I} = \frac{470 \times 10^{-6} \cdot 13.75}{85/15 \times 10^{-3}} = 11.4 s$$

**Step 3. Take an Assumption on Efficiency**

The efficiency  $\eta$  is usually assumed to be 90%. Then, the input power P<sub>in</sub> is 111 W. This input power will be frequently used in the next few design steps.

$$\eta = 90\%$$

$$P_{in} = \frac{P_{out}}{\eta} = \frac{100}{90\%} = 111 W$$

**Step 4. Calculate the Current Stress**

The worst case input current rating happens when input is 85 Vac. The input RMS current I<sub>ac</sub> is 1.31 Aac. The suffix ac denotes that it is RMS value. This current stress is mainly on the front-ended rectifier.

$$I_{ac} = \frac{P_{in}}{V_{ac}} = \frac{111}{85} = 1.31 Aac$$

The instantaneous maximum current stress in the PFC stage will be 3.7 A in critical mode.

$$I_{pk} = 2\sqrt{2} I_{ac} = 3.7 A$$

This current stress affects the component selections on the current sense resistor, MOSFET, diode, and inductor.

**Step 5. Oscillator Capacitor Design**

The switching frequency can be set by either oscillator mode or synchronization mode in the NCP1601. In this application, it is set at oscillator mode. Figure 34 in the NCP1601 data sheet shows that a 100 pF capacitor can set the frequency to 107 kHz. Actually, this frequency is only valid for the DCM operation because CRM is with a lower switching frequency. However, this frequency provides a reference on calculating the inductor for CRM in the next design step.

$$f = 107 \text{ kHz}$$

$$T = \frac{1}{f} = 9.35 \text{ } \mu\text{s}$$

**Step 6. Inductor Design**

The minimum CRM inductance  $L_{(CRM)}$  at low line is obtained as follows:

$$\begin{aligned} L_{(CRM)} &= \frac{V_{out} - V_{in}}{V_{out}} \frac{V_{in}}{I_{pk}} \frac{1}{f} \\ &= \frac{390 - \sqrt{2} \cdot 85}{390} \frac{\sqrt{2} \cdot 85}{3.7} \frac{1}{107 \times 10^3} = 210 \text{ } \mu\text{H} \end{aligned}$$

The maximum value of  $L_{(CRM)}$  is at low line. Hence, a value greater than  $L_{(CRM)}$  can make the circuit to operate in CRM. The inductor  $L$  is therefore set to be 230  $\mu\text{H}$ . The switching frequency is 99 kHz and it is in CRM.

$$L = 230 \text{ } \mu\text{H}$$

$$\begin{aligned} \text{freq} &= \frac{V_{out} - V_{in}}{V_{out}} \frac{V_{in}}{I_{pk}} \frac{1}{L} \\ &= \frac{390 - \sqrt{2} \cdot 85}{390} \frac{\sqrt{2} \cdot 85}{3.7} \frac{1}{230 \times 10^{-6}} = 98 \text{ kHz} < 107 \text{ kHz} \end{aligned}$$

**Step 7. Ramp Capacitor Design**

Maximum power can be obtained when  $V_{control} = 1 \text{ V}$ . Worst case is at low line 85 Vac.

$$\begin{aligned} C_{ramp} &> \frac{P_{in}}{V_{ac}^2} \cdot 2LI_{ch} \\ &= \frac{111}{85^2} \cdot 2 \cdot 230 \times 10^{-6} \cdot 100 \times 10^{-6} = 706 \text{ pF} \end{aligned}$$

There is a typical 20 pF background capacitance on the ramp pin in the NCP1601. The  $C_{ramp}$  is selected to be as small as possible to limit the maximum power transfer. Marginally, an external 680 pF capacitor is good enough for this application.

$$C_{ramp} = 680 \text{ pF}$$

With this value of  $C_{ramp}$ , the control voltage  $V_{control}$  in high line and low line condition are obtained.

In low line 85 Vac,

$$\begin{aligned} V_{control} &= \frac{2LI_{ch}P_{in}}{C_{ramp}V_{ac}^2} \\ &= \frac{2 \cdot 230 \times 10^{-6} \cdot 100 \times 10^{-6} \cdot 111}{(680 + 20) \times 10^{-12} \cdot 85^2} = 1.01 \text{ V} \end{aligned}$$

In high line 265 Vac,

$$\begin{aligned} V_{control} &= \frac{2LI_{ch}P_{in}}{C_{ramp}V_{ac}^2} \\ &= \frac{2 \cdot 230 \times 10^{-6} \cdot 100 \times 10^{-6} \cdot 111}{(680 + 20) \times 10^{-12} \cdot 265^2} = 0.1 \text{ V} \end{aligned}$$

**Step 8. Check the Switching Periods to Ensure CRM in the Sinusoidal Peaks**

In low line 85 Vac, the switching period ( $t_1 + t_2$ ) and MOSFET on time ( $t_1$ ) are as followed.

$$\begin{aligned} t_1 + t_2 &= \frac{V_{out}}{V_{out} - V_{in}} \frac{C_{ramp}V_{control}}{I_{ch}} \\ &= \frac{390}{390 - \sqrt{2} \cdot 85} \frac{700 \times 10^{-12} \cdot 1.01}{100 \times 10^{-6}} \\ &= 10.22 \text{ } \mu\text{s} > T \end{aligned}$$

$$t_1 = \frac{C_{ramp}V_{control}}{I_{ch}} = \frac{700 \times 10^{-12} \cdot 1.01}{100 \times 10^{-6}} = 7.07 \text{ } \mu\text{s}$$

In high line 265 Vac, the switching period ( $t_1 + t_2$ ) and MOSFET on time ( $t_1$ ) are as followed.

$$\begin{aligned} t_1 + t_2 &= \frac{V_{out}}{V_{out} - V_{in}} \frac{C_{ramp}V_{control}}{I_{ch}} \\ &= \frac{390}{390 - \sqrt{2} \cdot 265} \frac{700 \times 10^{-12} \cdot 0.1}{100 \times 10^{-6}} \\ &= 17.92 \text{ } \mu\text{s} > T \end{aligned}$$

$$t_1 = \frac{C_{ramp}V_{control}}{I_{ch}} = \frac{700 \times 10^{-12} \cdot 0.1}{100 \times 10^{-6}} = 0.7 \text{ } \mu\text{s}$$

As long as the switching period is larger than the DCM switching period  $T$ , the circuit operates in CRM and the maximum current stress is minimized.

**Step 9. Current Sense Resistors Design**

The settings of current sense resistor  $R_{CS}$  and sense resistor  $R_S$  defines the zero current threshold  $I_{L(ZCD)}$  and overcurrent protection threshold  $I_{L(OCP)}$  by the following two design equations.

$$I_{L(OCP)} = \frac{R_S \cdot 200 \text{ } \mu\text{A} - 3.2 \text{ mV}}{R_{CS}}$$

$$I_{L(ZCD)} = \frac{R_S \cdot 14 \mu A - 7.5 \text{ mV}}{R_{CS}}$$

Because the  $I_{L(ZCD)}$  has to be greater than zero,  $R_S$  has to be greater than  $535.7 \Omega$  which gives  $I_{L(ZCD)} > 0$ . When  $R_S$  is very close to  $535.7 \Omega$  (say  $R_S = 536 \Omega$ ),  $I_{L(OCP)} / I_{L(ZCD)} = 26000$  and  $I_{L(ZCD)}$  can be very small with a finite  $I_{L(OCP)}$ . For example, if the maximum stress is  $3.7 \text{ A}$ , then  $R_{CS}$  is  $28 \text{ m}\Omega$  and  $I_{L(ZCD)}$  is  $143 \mu\text{A}$ .

$$R_{CS} = \frac{R_S \cdot 200 \mu A - 3.2 \text{ mV}}{I_{L(OCP)}} = \frac{536 \cdot (200 \times 10^{-6}) - 0.0032}{3.7} = 0.028 \Omega$$

$$I_{L(ZCD)} = \frac{R_S \cdot 14 \mu A - 7.5 \text{ mV}}{R_{CS}} = \frac{536 \cdot (14 \times 10^{-6}) - 0.0075}{0.028} = 143 \mu\text{A}$$

However, tolerance exists in real world and the actual design can only be closed to this one.

When the value of  $R_{CS}$  is  $0.05 \Omega$ , its power dissipation  $P_d$  is  $129 \text{ mW}$ .

$$R_{CS} = 0.05 \Omega$$

$$P_d = I_{ac}^2 \cdot R_{CS} \cdot 1.5 = 1.312^2 \cdot 0.05 \cdot 1.5 = 129 \text{ mW}$$

In order to have  $I_{L(OCP)} = 3.7 \text{ A}$ , the  $R_S$  will be  $941 \Omega$ .

$$R_S = \frac{R_{CS} \cdot I_{L(OCP)} + 3.2 \text{ mV}}{200 \mu A} = \frac{0.05 \cdot 3.7 + 0.0032}{(200 \times 10^{-6})} = 941 \Omega$$

$941 \Omega$  is not a standard size of a resistor. If the  $R_S$  is  $1 \text{ k}\Omega$  then  $I_{L(OCP)}$  and  $I_{L(ZCD)}$  are also obtained.

$$R_S = 1 \text{ k}\Omega$$

$$I_{L(OCP)} = \frac{R_S \cdot 200 \mu A - 3.2 \text{ mV}}{R_{CS}} = \frac{1000 \cdot (200 \times 10^{-6}) - 0.0032}{0.05} = 3.936 \text{ A}$$

$$I_{L(ZCD)} = \frac{R_S \cdot 14 \mu A - 7.5 \text{ mV}}{R_{CS}} = \frac{1000 \cdot (14 \times 10^{-6}) - 0.0075}{0.05} = 130 \text{ mA}$$

**Step 10. Output Capacitor Design**

The choice of output capacitance is usually dictated by the required hold-up time or the acceptable output ripple voltage for a given application. As a rule of thumb, output capacitance is generally set at  $1 \mu\text{F}/\text{W}$ . Hence, a  $100 \text{ W}$  application needs  $100 \mu\text{F}$  output capacitance.


$$C = 100 \mu\text{F}$$

The hold-up time  $t_{HOLD}$  which is the time a power supply needs to maintain its voltage with the specified range after a dropout of the line voltage.

$$C = \frac{2P_{out} \cdot t_{HOLD}}{V_{out\_min}^2 - V_{OP\_min}^2}$$

where  $V_{out\_min}$  is the minimum value of the regulated output voltage at full load and  $V_{op\_min}$  is the minimum input voltage of the driven load of the PFC. Because there is no particular specification on the hold-up time, this term is not further studied here.

The major output ripple component in a PFC circuit is usually its rectified line frequency because it cannot be easily filtered out by inductors and capacitors. The CCM or DCM operations mainly affect the switching frequency ripple which is always much smaller than the rectified line frequency ripple and hence generally neglected.

 


**Figure 4. Low-Frequency Equivalent Circuit of the Output Stage**

The low frequency output stage of a PFC stage can be simplified into Figure 4. The line frequency current source is a rectified sinusoidal (if only low frequency is considered) and its rms value  $I_{out(rms)}$  is simply  $P_{out}/V_{out}$ . Hence, peak-to-peak value  $I_{out(pk-pk)}$  is as follow:

$$I_{out(pk-pk)} = \sqrt{2} I_{out(rms)} = \frac{\sqrt{2} P_{out}}{V_{out}} = \frac{\sqrt{2} 100}{390} = 0.363 \text{ A}$$

Now that the capacitor is the only energy storage media in the circuit in Figure 4 and the discharging time is one-fourth of the line frequency as shown in Figure 5.

 

**Figure 5. Output Voltage Ripple**

Hence, the low frequency output ripple can be obtained as following:

$$dv = \frac{Idt}{C} = \frac{0.354 \cdot \frac{1}{4} \cdot \frac{1}{50}}{100 \times 10^{-6}} = 17.7 \text{ V}$$

For the sake of safety, 450 V rating output capacitor is always recommended if the nominal output voltage of the circuit is 400 V.

On the other hand, in a NCP1601 PFC circuit the instantaneous output voltage affects the instantaneous control voltage  $V_{control}$ . If the output voltage ripple is too high, it will make a large ripple on control voltage and the power factor can be dramatically reduced for highly dynamic control voltage.

**Step 11. Input Filter Design**

CRM and/or DCM PFC circuit needs an input filtering circuit to bypass the high frequency current so that the input current consists of the low frequency part only. The simplest filtering circuit is a capacitor  $C_F$  across the input lines in Figure 6. An input impedance  $Z_{in}$  is assumed to be with the input AC source but the value of the input impedance is usually unavailable and negligible in most of the application. Hence, a differential mode filtering inductor  $L_F$  is added in the calculation of the currents in Figure 6. This differential mode inductor usually exists in the form of common mode inductors.

 


Figure 6. Filtering Capacitor Circuit

 


Figure 7. High-Frequency Equivalent Circuit and Phasor Diagram

The high frequency source in Figure 6 is the inductor current  $I_L$ . A high frequency equivalent circuit of Figure 6 is shown in Figure 7. Therefore, the phasor diagram is drawn

and the percentage of the high frequency current ( $I_L$ ) getting into the input side ( $I_{in}$ ) is as follows.

$$\begin{aligned} \frac{I_{in}}{I_L} &= \frac{1/(2\pi f C_F)}{2\pi f L_F - 1/(2\pi f C_F)} = \frac{1}{4\pi^2 f^2 L_F C_F - 1} \\ &= \frac{1}{4\pi^2 \cdot \left(\frac{1}{11.10 \times 10^{-6}}\right)^2 \cdot 1000 \times 10^{-6} \cdot 1 \times 10^{-6} - 1} \\ &= 0.31\% \end{aligned}$$

when  $L_F = 1 \text{ mH}$  and  $C_F = 1 \mu\text{F}$ .

On the other hand, the addition of the filtering capacitor  $C_F$  also draws a low frequency (i.e., line frequency  $f_L$ ) current  $I_F$  in Figure 8. It increases the overall magnitude of the input current  $I_{in}$  for the same power  $I_L$ . The low frequency equivalent circuit of Figure 6 is shown in Figure 8. The equivalent resistance  $R_{eq}$  is the PFC circuit equivalent resistance which can be modeled to be purely resistive for its PFC property and  $R_{eq}$  is expressed as follows.

$$R_{eq} = \frac{V_{in}^2}{P_{in}} = \frac{V_{in}^2 \cdot \eta}{P_{out}}$$

 


Figure 8. Low-Frequency Equivalent Circuit and Phasor Diagram

Therefore, the percentage of the increase of the input current due to the addition of the filtering capacitor is obtained.

$$\begin{aligned} \frac{I_{in}}{I_L} &= \sqrt{1 + \left(\frac{R_{eq}}{1/(2\pi f_L C_F)}\right)^2} = \sqrt{1 + \left(\frac{V_{in}^2 \eta 2\pi f_L C_F}{P_{out}}\right)^2} \\ &= \sqrt{1 + \left(\frac{265^2 \cdot 0.9 \cdot 2 \cdot \pi \cdot 50 \cdot 1 \times 10^{-6}}{100}\right)^2} \\ &= 101.95\% \end{aligned}$$

### Step 12. Layout Design

Figures 9 and 10 illustrate the layout of the 100 W circuit. As one of the layout rules, the control circuit is located at a corner of the PCB to prevent any unwanted high frequency noise from the main power switching circuit. The NCP1601A is associated with a bunch of pF order capacitors which are very sensitive. The best way to handle them is to minimize the PCB trace distance. Hence, this bunch of pF capacitors are ideally located at the bottom layer of the NCP1601A.

The PCB trace connected to the low impedance current sense resistor is a major source of noise or error. It is recommended to minimize this PCB trace distance. Finally, the circuit is layout in a single PCB layer board. As a result, a 10  $\Omega$  resistor is added between the MOSFET gate and the NCP1601A output. This circuit path provides a large amount of high current ac noise so that the nearby trace on the output feedback is easily polluted. Hence, some surface mounted decoupling capacitors are located there for the noise.



# AND8182/D

 


Figure 9. Demo Circuit Top Layer Layout

 


Figure 10. Demo Circuit Bottom Layer Layout

**Step 13. Fine Tuning Capacitor on  $V_{control}$  Pin**

The unity power factor in the NCP1601 PFC circuit greatly relies on how steady the control voltage in the  $V_{control}$  pin (pin 2). A large external capacitor on this pin can help to reduce the noise and dynamics of this voltage and give a decent power factor. However, if the capacitor is too large, it will reduce the dynamic response or startup transient of the circuit.

**MEASUREMENT**

The performance of the example PFC circuit is listed in Table 2. The waveforms with different input voltages are

also shown in Figures 11 to 14. In Figures 11 to 14, the upper trace is the input current with 1 A/div. The center trace is the output voltage with 100 V/div. And the lower trace is the boost input voltage with 100V/div. The output voltage of the circuit is set by a  $(1.8\text{ M}\Omega + 150\text{ k}\Omega) \times 200\text{ }\mu\text{A} = 390\text{ V}$ . There is roughly 374 V ( $96\% \times 390$ ) to 390 V (100%) regulation window in the NCP1601. It explains the variation of the output voltage over the wide input range in Table 2. The THD can be improved by 2 or 3% if the front-ended 1  $\mu\text{F}$  capacitor is reduced.

**Table 2. Experimental Measurement of the Circuit.**

Input	Output	Efficiency	PF/THD
85 Vac 108.2 W	370.5 V 100.8 W	93.17%	0.995 / 8.3%
110 Vac 107.9 W	384.8 V 101.2 W	93.83%	0.991 / 12.8%
120 Vac 105.8 W	385.2 V 99.8 W	94.33%	0.990 / 11.3%
180 Vac 104.6 W	391.2 V 99.8 W	95.41%	0.975 / 11.9%
220 Vac 104.7 W	394.2 V 100.1 W	95.63%	0.952 / 16.7%
230 Vac 104.4 W	394.8 V 100.3 W	96.05%	0.945 / 21.1%
265 Vac 104.6 W	400.9 V 100.5 W	96.08%	0.901 / 38.9%

 


Figure 11. 85 Vac Input Voltage

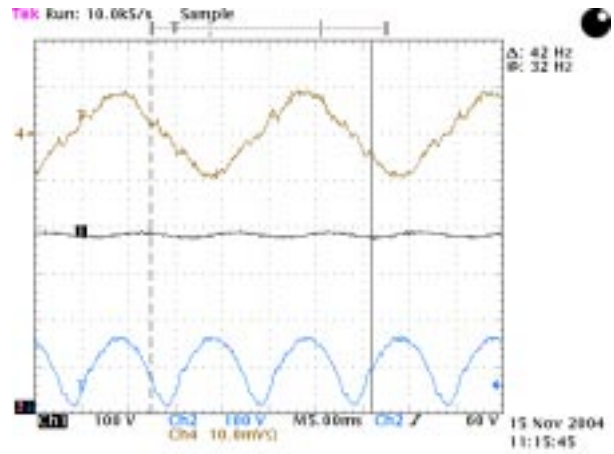


Figure 12. 115 Vac Input Voltage

 


Figure 13. 230 Vac Input Voltage

 


Figure 14. 265 Vac Input Voltage



## AND8182/D

In order to illustrate the capability of both DCM and CRM operation of the NCP1601, Figures 15 to 17 are taken. The upper trace of the figures is the boost input voltage with 100 V/div. The lower trace is the voltage across the 0.05  $\Omega$  current sense resistor with 50 mV/div so that the inductor current and the mode of operation are indirectly shown. Figure 15 shows the traces with 2 ms time base so that the maximum and minimum value of the boost input voltage is

observed in this time base but the voltage across the current sense resistor is too noisy to study. Figure 16 shows the moment when the boost input voltage is the maximum. It illustrates that the circuit is in CRM operation in this moment. Figure 17 shows the moment when the boost input voltage is the minimum. It illustrates that the circuit is in DCM operation.

 


Figure 15. Current Sense Resistor Voltage

 


Figure 16. CRM Operation in Near the Peak

 


Figure 17. DCM Operation in the Zero Crossing

## AND8182/D

### CONCLUSION

A 100 W example circuit using NCP1601A is presented. The design steps and measurement are covered. It is noted that the NCP1601 can perform a decent power factor

correction and efficiency in CRM and DCM so that it is suitable for low power PFC applications. Major equations for the NCP1601 design are listed in appendix for reference.

### Appendix I – Bill of Material of the NCP1601 100 W / 390 V Example Circuit

Qty	Part No.	Description	Manufacturer
1	NCP1601A	PFC Controller	ON Semiconductor
4	1N5406	Standard Diode, 4 A 600 V	ON Semiconductor
2	1N4001	Standard Diode, 1 A 50 V	ON Semiconductor
1	MUR460	Fast Recovery Diode, 4 A 600 V	ON Semiconductor
1	MZP4745A	Zener Diode, 16 V 5%	ON Semiconductor
1	PCV-2-105-02	Inductor, 1000 $\mu$ H / 2 A	Coilcraft
1	CTX22-16885	Custom Transformer, $L_p = 230 \mu$ H / 6 A, 25:1:1	Cooper Coiltronics
1	SPP07N60C3	650 V, 0.6 $\Omega$ TO-220AB N-Channel MOSFET	Infineon
2	RE105	Noise Suppression Capacitor	Okaya
2	50MH71M4X7	Aluminum Electrolytic Capacitor, 1 $\mu$ F 50 V	Rubycon
1	UHD1E471MPD	Aluminum Electrolytic Capacitor, 470 $\mu$ F 25 V	Nichicon
1	450AXW100M18X40	Aluminum Electrolytic Capacitor, 100 $\mu$ F 450 V	Rubycon
1	VJ1206A101KXAA	1206 SMD Capacitor, 100 pF	Vishay
1	VJ1206Y154KXXA	1206 SMD Capacitor, 0.15 $\mu$ F	Vishay
1	VJ1206A681KXAA	1206 SMD Capacitor, 680 pF	Vishay
1	VJ1206A102KXAA	1206 SMD Capacitor, 1000 pF	Vishay
1	WSL2010-R0500-F	SMD Resistor, 0.05 $\Omega$ 1 W 1%	Vishay Dale
1		Axial Resistor, 150 k $\Omega$ 1/2 W	
1		Axial Resistor, 1.8 M $\Omega$ 1/4 W	
1		Axial Resistor, 150 k $\Omega$ 1/4 W	
1		Axial Resistor, 1 k $\Omega$ 1/4 W	
1		Axial Resistor, 10 $\Omega$ 1/4 W	
2	26-60-4030 or 009652038	Male Header	Molex

Appendix II – Summary of Equations in NCP1601 Boost PFC

Description	Critical Mode (CRM)	Discontinuous Mode (DCM)
Boost converter	$\frac{V_{out}}{V_{in}} = \frac{t_1 + t_2}{t_2}$ $\rightarrow \frac{V_{out} - V_{in}}{V_{out}} = \frac{t_1}{t_1 + t_2}$	$\frac{V_{out}}{V_{in}} = \frac{t_1 + t_2}{t_2}$ $\rightarrow \frac{V_{out} - V_{in}}{V_{out}} = \frac{t_1}{t_1 + t_2}$
Input current averaged by filter capacitor	$I_{in} = \frac{I_{pk}}{2}$	$I_{in} = \frac{t_1 + t_2}{T} \frac{I_{pk}}{2}$
Voltage for on time $V_{ton}$	$V_{ton} = V_{control}$	$V_{ton} = \frac{T}{t_1 + t_2} V_{control}$
MOSFET on-time $t_1$	$t_1 = \frac{L I_{pk}}{V_{in}}, \text{ or } t_1 = \frac{C_{ramp} V_{control}}{I_{ch}}$ $\rightarrow t_1 \text{ is constant for unity PFC}$ $\rightarrow V_{control} \text{ is constant for unity PFC}$	$t_1 = \frac{L I_{pk}}{V_{in}}, \text{ or } t_1 = \sqrt{\frac{V_{out} - V_{in}}{V_{out}}} \frac{T C_{ramp} V_{control}}{I_{ch}}$ $\rightarrow t_1 (t_1 + t_2) \text{ is constant for unity PFC}$ $\rightarrow V_{control} \text{ is constant for unity PFC}$
Switching period	$t_1 + t_2 = \frac{V_{out}}{V_{out} - V_{in}} \frac{C_{ramp} V_{control}}{I_{ch}}, \text{ or}$ $t_1 + t_2 = \frac{V_{out}}{V_{out} - V_{in}} \frac{L I_{pk}}{V_{in}}$	$t_1 + t_2 = \frac{T C_{ramp} V_{control}}{t_1 I_{ch}}, \text{ or}$ $t_1 + t_2 = \sqrt{\frac{V_{out}}{V_{out} - V_{in}}} \frac{T C_{ramp} V_{control}}{I_{ch}}$
Minimum Inductor for CRM	$L > L_{(CRM)} = \frac{V_{out} - V_{in}}{V_{out}} \frac{V_{in}}{I_{pk}} \frac{1}{f}$	Same as CRM
Input impedance	$Z_{in} = \frac{2L I_{ch}}{C_{ramp} V_{control}}$	Same as CRM
Input power	$P_{in} = \frac{V_{ac}^2 C_{ramp} V_{control}}{2L I_{ch}}$	Same as CRM
Output power	$P_{out} = \eta P_{in} = \frac{\eta V_{ac}^2 C_{ramp} V_{control}}{2L I_{ch}}$	Same as CRM
Maximum input power when $V_{control} = 1 \text{ V}$	$P_{in\_max} = \frac{V_{ac}^2 C_{ramp}}{2L I_{ch}}$	Same as CRM
Minimum ramp capacitor when $V_{control} = 1 \text{ V}$	$C_{ramp} > \frac{P_{in}}{V_{ac}^2} \cdot 2L I_{ch}$	Same as CRM
Control voltage $V_{control}$	$V_{ctrl} = \frac{2L I_{ch} P_{in}}{C_{ramp} V_{ac}^2}$	Same as CRM

**ON Semiconductor** and  are registered trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer. This literature is subject to all applicable copyright laws and is not for resale in any manner.

## PUBLICATION ORDERING INFORMATION

### LITERATURE FULFILLMENT:

Literature Distribution Center for ON Semiconductor  
P.O. Box 61312, Phoenix, Arizona 85082-1312 USA  
**Phone:** 480-829-7710 or 800-344-3860 Toll Free USA/Canada  
**Fax:** 480-829-7709 or 800-344-3867 Toll Free USA/Canada  
**Email:** [orderlit@onsemi.com](mailto:orderlit@onsemi.com)

**N. American Technical Support:** 800-282-9855 Toll Free  
USA/Canada

**Japan:** ON Semiconductor, Japan Customer Focus Center  
2-9-1 Kamimeguro, Meguro-ku, Tokyo, Japan 153-0051  
**Phone:** 81-3-5773-3850

**ON Semiconductor Website:** <http://onsemi.com>

**Order Literature:** <http://www.onsemi.com/litorder>

For additional information, please contact your  
local Sales Representative.